



CI's $U_1(t) = U_0$
 $U_2(t) = 0$

1) On a $C_1 \dot{U}_1 = -C_2 \dot{U}_2$

donc $C_1 U_1 = -C_2 U_2 + \text{cte}$ CI's $C_1 U_0 = 0 + \text{cte}$

In fine $C_1 U_1 = -C_2 U_2 + C_1 U_0$

2) LDM: $0 = RC_1 \dot{U}_1 + U_1 - U_2$ or $U_2 = \frac{C_1}{C_2} (U_0 - U_1)$

ie $RC_1 \dot{U}_1 + U_1 + \frac{C_1}{C_2} U_1 = \frac{C_1}{C_2} U_0$

$\dot{U}_1 + \frac{C_1 + C_2}{RC_1 C_2} U_1 = \frac{U_0}{RC_2}$

$U_1 = U_{1sh} + U_{1sp}$

" $Ae^{-t/\tau}$
 $\rightarrow 0$

" $\frac{C_1}{C_1 + C_2} U_0$

CI's DC2!

3) Energie initiale: unchg = ds C_1

$E_0 = \frac{1}{2} C_1 U_0^2$

Energie finale stockée dans C_1 ET dans C_2

$C_1: \frac{1}{2} C_1 U_{DC}^2 = \frac{1}{2} C_1 \left(\frac{C_1}{C_1 + C_2} U_0 \right)^2 = \frac{1}{2} \frac{C_1^3}{(C_1 + C_2)^2} U_0^2$

$C_2: \frac{1}{2} C_2 U_{DC}^2 = \frac{1}{2} C_2 \left(\frac{C_1}{C_1 + C_2} U_0 \right)^2 = \frac{1}{2} \frac{C_1^2 C_2}{(C_1 + C_2)^2} U_0^2$

Total: $E_f = \frac{1}{2} \frac{C_1^3 + C_1^2 C_2}{(C_1 + C_2)^2} U_0^2 = \frac{1}{2} C_1^2 \frac{C_1 + C_2}{(C_1 + C_2)^2} U_0^2$

$= \frac{1}{2} \left(\frac{C_1}{C_1 + C_2} \right)^2 U_0^2$

\Rightarrow La \neq d'énergie entre E_0 et E_f est perdue en effet Joule:

$\Delta E_{\text{Joule}} = E_0 - E_f = \frac{1}{2} C_1 U_0^2 - \frac{1}{2} \left(\frac{C_1}{C_1 + C_2} \right)^2 U_0^2 = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} U_0^2$